 


→ we use the clock to trigger transitions across many elements in sync. circuit

→ during a clock cycle, combinational logic blocks compute the next state (also known as next-state logic)

→ in the timing chapter, you will see how important it is for a clock cycle to be longer than any combinational delay (computing)

reason why we use flip-flops and not latches in sequential circuits:




(this is for a D latch)

FSM: Discrete time-model of a stateful system

It contains:

 - a finite number of states
- a finite number of external inputs
- a finite number of external outputs
- a specification of all state transitions
- a specification of how external outputs are determined



← parts

→ The state register(s) store the current state and output the next state at the rising edge (only sequential circuit)

→ Combinational circuits: Next state logic and output logic

Moore machines: outputs depend on current state only

Meady machines: outputs also depend on current inputs

FSM design (crucial for exam!):

1. Identify your inputs/outputs

2. Draw your state transition diagram

→ start with the reset state and what is caused by it

→ add states and transitions

→ this is similar to programming

→ FSMs have a sequential control flow (conditionals, jumps)

→ if/else construct controlled by inputs → outputs controlled by state or inputs

3. Moore machine: write state transition table, write output table


Meady machine: write state transition and output table (combined)

4. Select state encodings:


Binary (full) encoding: Use minimum possible number of bits →  $\log_2(\# \text{states})$  bits  
→ Example: 00, 01, 10, 11  
→ minimizes # flip-flops, not necessarily output logic

One-hot encoding: one bit for every state → #states bits needed → example: 0001, 0010, 0100, 1000  
→ simple, automatable, doesn't need much next state logic, but inefficient for flip-flops

 Output encoding: directly encode outputs in state



(a) (Moore)

 

(b) (Mealy)

→ example: 001, 010, 100, 110 for a traffic light (Only works for Moore type)

5. Write Boolean equations for next state and output logic

6. Sketch the circuit (this is formally, you won't have to do this)

Simple example:

■ "Smart" traffic light controller

□ 2 inputs:


■ Traffic sensors:  $T_A, T_B$  (TRUE when there's traffic)

□ 2 outputs:

■ Lights:  $L_A, L_B$  (Red, Yellow, Green)


□ State changes every 5 seconds

 ■ Except if green and traffic, stay green



■ Inputs: CLK, Reset,  $T_A, T_B$




■ Outputs:  $L_A, L_B$

 

■ Moore FSM: outputs labeled in each state


□ States: Circles

□ Transitions: Arcs

   

| Current State |       | Inputs |       | Next State |        |
|---------------|-------|--------|-------|------------|--------|
| $S_1$         | $S_0$ | $T_A$  | $T_B$ | $S'_1$     | $S'_0$ |
| 0             | 0     | 0      | X     | 0          | 1      |
| 0             | 0     | 1      | X     | 0          | 0      |
| 0             | 1     | X      | X     | 1          | 0      |
| 1             | 0     | X      | 0     | 1          | 1      |
| 1             | 0     | X      | 1     | 1          | 0      |
| 1             | 1     | X      | X     | 0          | 0      |


| State | Encoding |
|-------|----------|
| S0    | 00       |
| S1    | 01       |
| S2    | 10       |
| S3    | 11       |

 

| Current State |       | Inputs |       | Next State |        |
|---------------|-------|--------|-------|------------|--------|
| $S_1$         | $S_0$ | $T_A$  | $T_B$ | $S'_1$     | $S'_0$ |
| 0             | 0     | 0      | X     | 0          | 1      |
| 0             | 0     | 1      | X     | 0          | 0      |
| 0             | 1     | X      | X     | 1          | 0      |
| 1             | 0     | X      | 0     | 1          | 1      |
| 1             | 0     | X      | 1     | 1          | 0      |
| 1             | 1     | X      | X     | 0          | 0      |

| State | Encoding |
|-------|----------|
| S0    | 00       |
| S1    | 01       |
| S2    | 10       |
| S3    | 11       |
 
$$S'_1 = (\overline{S_1} \cdot S_0) + (S_1 \cdot \overline{S_0} \cdot T_B) + (S_1 \cdot \overline{S_0} \cdot T_B)$$




| Current State |       | Inputs |       | Next State |        |
|---------------|-------|--------|-------|------------|--------|
| $S_1$         | $S_0$ | $T_A$  | $T_B$ | $S'_1$     | $S'_0$ |
| 0             | 0     | 0      | X     | 0          | 1      |
| 0             | 0     | 1      | X     | 0          | 0      |
| 0             | 1     | X      | X     | 1          | 0      |
| 1             | 0     | X      | 0     | 1          | 1      |
| 1             | 0     | X      | 1     | 1          | 0      |
| 1             | 1     | X      | X     | 0          | 0      |

| State | Encoding |
|-------|----------|
| S0    | 00       |
| S1    | 01       |
| S2    | 10       |
| S3    | 11       |


$$S'_1 = S_1 \text{ xor } S_0 \quad (\text{Simplified})$$
 
$$S'_0 = (\overline{S_1} \cdot \overline{S_0} \cdot \overline{T_A}) + (S_1 \cdot \overline{S_0} \cdot T_B)$$



| Current State |       | Outputs |        |
|---------------|-------|---------|--------|
| $S_1$         | $S_0$ | $L_A$   | $L_B$  |
| 0             | 0     | green   | red    |
| 0             | 1     | yellow  | red    |
| 1             | 0     | red     | green  |
| 1             | 1     | red     | yellow |

| Output | Encoding |
|--------|----------|
| green  | 00       |
| yellow | 01       |
| red    | 10       |

 

| Current State |       | Outputs  |          |          |          |
|---------------|-------|----------|----------|----------|----------|
| $S_1$         | $S_0$ | $L_{A1}$ | $L_{A0}$ | $L_{B1}$ | $L_{B0}$ |
| 0             | 0     | 0        | 0        | 1        | 0        |
| 0             | 1     | 0        | 1        | 1        | 0        |
| 1             | 0     | 1        | 0        | 0        | 0        |
| 1             | 1     | 1        | 0        | 0        | 1        |

| Output | Encoding |
|--------|----------|
| green  | 00       |
| yellow | 01       |
| red    | 10       |


$$L_{A1} = S_1$$

$$L_{A0} = \overline{S_1} \cdot S_0$$

$$L_{B1} = \overline{S_1}$$


$$L_{B0} = S_1 \cdot S_0$$

Schematic:

 
 
## Practical Exam Example:

Note: I see it as very unlikely that you will have to draw up a schematic, everything else is important!  
from FS22:



outputs: idle 0  $\rightarrow$  10, idle 1  $\rightarrow$  10, transit  $\rightarrow$  00,  
unload 1  $\rightarrow$  01, unload 2  $\rightarrow$  01, emergency  $\rightarrow$  11

## 2 Finite State Machines [50 points]

The Polybahn from Central to Polyterasse has broken down! To fix it you need to design a finite state machine that controls the Polybahn's two doors *A* and *B*.

The Polybahn should operate as follows:

- Initially the Polybahn is empty and **idle**, and passengers can enter through door *A*.
- The Polybahn is full when it carries 2 passengers.
- When it is full and idle, the Polybahn goes into **transit** to the other station with both doors closed.
- After reaching the station, the Polybahn will **unload** all passengers through door *B*, while door *A* is still closed.
- After the last passenger has exited the Polybahn, door *B* closes and the Polybahn becomes **idle**.
- Should (1) a passenger fall out of the Polybahn during **transit**, or (2) the Polybahn become overfull ( $\geq 3$  passengers) at any point, it stops in **emergency** mode, where it opens all doors and remains (unless reset to the initial **idle** state).

The FSM receives two input bits, with the following meaning:

| Input | Meaning                           |
|-------|-----------------------------------|
| 00    | no change                         |
| 01    | exactly one passenger left        |
| 10    | exactly one passenger entered     |
| 11    | the Polybahn arrived in a station |

The FSM produces two output bits: The first bit, *A*, holds door *A* open when it is 1. The second bit, *B*, holds door *B* open when it is 1.

- (a) [25 points] Complete the Moore-type FSM below by (1) drawing the transition edges between the states (including reset), (2) specifying the edges' respective input bits, and (3) specifying the output bits of each state. Any input for which no outgoing edge is specified is assumed as a self loop. The 6 given states are sufficient, do not draw additional states.  
Note: Passengers sometimes slip in or out through incorrect doors, or even through closed doors. Your FSM must correctly handle such cases.


## Timing:

## Electrical Basics:

lowest voltage in a system  $\rightarrow$  ground/GND (usually 0V)

highest voltage in a system  $\rightarrow$   $V_{DD}$ , comes from PSU

## Logic Levels:

 

$\rightarrow$  first gate: driver / second gate: receiver

$\rightarrow$  driver produces logical LOW (0)  $\rightarrow$  output between 0 and  $V_{OL}$  (output low)  
HIGH (1)  $\rightarrow$  output between  $V_{OH}$  and  $V_{DD}$  (output high)

$\rightarrow$  receiver gets input between 0 and  $V_{IL}$   $\rightarrow$  reads logical LOW (input low)  
 $V_{IH}$  and  $V_{DD}$   $\rightarrow$  reads logical HIGH (input high)

$\rightarrow$  forbidden zone: between  $V_{IL}$  and  $V_{IH}$  (caused by defects or noise)


$\rightarrow$  Noise Margins:  $NM_L = V_{IL} - V_{OL}$  (low margin)  
 $NM_H = V_{OH} - V_{IH}$   $\rightarrow$  reasoning: we need output high  $>$  input high to correctly interpret outputs (with noise)  
output low  $<$  input low

→ Static Discipline: to avoid forbidden zone → given a log. valid input, any circuit element produces log. valid outputs

→ we can arbitrarily choose  $V_{DD}$ , but communicating gates must have compatible logic levels

→ we group gates into logic families like CMOS → all gates in CMOS adhere to static discipline with each other

 Combinational Timing: we want to optimize the speed of a circuit




→ Input change and output change have a delay for any circuit element

→ timing diagrams like this show the transient response of circuits

→ rising edge → logic LOW → HIGH, falling edge → logic HIGH → LOW

→ blue arrow indicates that rising edge of A causes rising edge of Y

 → delay is measured from 50% point (when signal is 50% between LOW/HIGH) of input to 50% point of output



$t_{pd}$  → propagation delay → max. time from the input change to the output's final value

$t_{cd}$  → contamination delay → max. time from the input change to the output value change

Critical path: slowest path with the most changes

Short path: fastest path with the least changes

 


Figure 2.69 Critical and short path waveforms

→ propagation delay of combinational circuit: sum of  $t_{pd}$  on critical path

→ contamination delay of comb. circuit: sum of  $t_{cd}$  on short path

Glitches: single input transition causes multiple output transitions

 


Figure 2.75 Circuit with a glitch

→ short path goes through AND and OR

→ critical goes through AND, OR, NOT

→ falling edge on B →  $n_2$  falls on short path before  $n_1$  rises on crit.

→ until  $n_1$  rises, two inputs to OR gate are 0 → Y drops to 0

→ when  $n_1$  does rise → Y comes back to 1 → that was our glitch

→ glitches are fine when we wait for  $t_{pd}$  before using the output, but here, we could prevent it by adding a <sup>redundant</sup> gate


Sequential Timing: remember how in a flip-flop, D is sampled on the clock edge?

→ an apt comparison to what happens in circuits is how you have to hold a camera still for a while before a shot and after (aperture time) → our aperture time consists of the <sup>( $t_{setup}$ )</sup> setup and <sup>( $t_{hold}$ )</sup> hold time

→ sequential circuits have a clock-to-Q contamination ( $t_{cq}$ ) and propagation ( $t_{pcq}$ )

delay → similar to combinational circuits, they are the fastest and slowest delays

 → for the circuit to sample its input correctly, the input must have been stable for  $t_{setup}$





before the clock edge and hold after  $\Rightarrow$  aperture time =  $t_{\text{setup}} + t_{\text{hold}}$

Dynamic Discipline: the inputs of a sync. circuit must be stable during the aperture time

$\rightarrow$  sample inputs that are not changing

System Timing: clock period  $T_c$  = time between rising edges of a clock,  $1/T_c = f_c \rightarrow$  clock frequency, which is measured in Hz (cycles per second)

$\rightarrow$  in this image, we try to calculate the clock period

$\rightarrow$   $R_1$  produces  $Q_1$  on the rising edge, they go through a block of comb. logic that produces  $D_2$  which goes to  $R_2$

$\rightarrow$  gray arrows  $\rightarrow$  contamination delay, blue arrows  $\rightarrow$  propagation delay

Setup Time Constraint:

$\rightarrow$   $D_2$  must be settled no later than before  $t_{\text{setup}}$

$\rightarrow$  we know that  $T_c \geq t_{\text{pcq}} + t_{\text{pd}} + t_{\text{setup}} \rightarrow$  can be rearranged to  $t_{\text{pd}} \leq T_c - (t_{\text{pcq}} + t_{\text{setup}})$

sequencing overhead

this equation is called setup time constraint,

because the comb. logic block cannot meaningfully compute  $D_2$  during  $t_{\text{pcq}}$  and  $t_{\text{setup}}$

$\rightarrow$  if  $t_{\text{pd}}$  is too long,  $D_2$  may not be at its final value when needed  $\rightarrow$  malfunction  $\rightarrow$  solution: increase  $T_c$  or redesign CL

Hold Time Constraints:

depends on manufacturers dictated internally

$\rightarrow$  the designer usually doesn't have control over  $t_{\text{ccq}}$ ,  $t_{\text{pcq}}$ ,  $t_{\text{hold}}$ ,  $t_{\text{setup}}$ , or  $T_c$

$\rightarrow$  hold time constraint:  $D_2$  must not change for  $t_{\text{hold}}$  after rising edge, but it

can change  $t_{\text{ccq}} + t_{\text{cd}}$  after rising edge  $\Rightarrow t_{\text{ccq}} + t_{\text{cd}} \geq t_{\text{hold}}$

$\Rightarrow t_{\text{cd}} \geq t_{\text{hold}} - t_{\text{ccq}}$

$t_{\text{ccq}}$  and  $t_{\text{hold}}$  outside our control

Example: 2 flip-flops: no comb. logic between  $\rightarrow t_{\text{hold}} \leq t_{\text{ccq}}$ , in practice,  $t_{\text{hold}} = 0$   
(or any chain of seq. logic elements)


$\rightarrow$  hold time violations cannot be fixed without redesigning the circuit (by increasing contamination delay)  $\rightarrow$

cannot be fixed by adjusting clock period  $\rightarrow$  very serious for real circuits

Clock skew (this came up in the lecture, so we must examine it)


$\rightarrow$  clock edges may vary (clock skew), caused by differing clock-register wire length, noise, and using both gated and ungated clocks

 $\rightarrow$  here,  $\text{CLK}_2$  is early because of the routing of the clock wire between  $R_1$  and  $R_2$



$\rightarrow$  clock may arrive up to  $t_{\text{skew}}$  earlier


 
$\rightarrow$  effect on setup time constraint:



→ worst case:  $R_1$  receives latest skewed clock,  $R_2$  receives earliest skewed clock because comb. logic propagation has least time

→ data still has to setup and propagate before sampling  $\Rightarrow T_c \geq t_{pcq} + t_{pd} + t_{setup} + t_{skew}$   
 $\Rightarrow t_{pl} \leq T_c - (t_{pcq} + t_{setup} + t_{skew}) \rightarrow$  skew added to constraint

Effect on hold time constraint:

  

→ worst case:  $R_1$  gets earliest skewed clock,  $R_2$  receives latest skewed clock

$\Rightarrow$  data must not arrive until hold time after late clock

$\Rightarrow t_{pcq} + t_{cd} \geq t_{hold} + t_{skew} \Rightarrow t_{cd} \geq t_{hold} + t_{skew} - t_{pcq}$

→ overall, clock skew increases both setup and hold time

Metastability: result of violating dyno. discipline <sup>(in flip-flops)</sup>  $\Rightarrow$  output can take on voltage between 0 and  $V_{DD}$  in forbidden zone  $\rightarrow$  metastable state

→ flip-flop will resolve output to 1 or 0, but resolution time is unbounded

Resolution time: when a flip-flop input changes at random time during clock cycle,  $t_{res}$  (resolution time is a random variable) (Aww flashbacks! 📺)

→ input changes outside aperture  $\rightarrow t_{res} = t_{pcq}$ , input changes within aperture  $\rightarrow t_{res}$  can be longer

Equation for  $t$  substantially longer than  $t_{pcq} \rightarrow P(t_{res} > t) = \frac{T_0}{T_c} e^{-\frac{t}{\tau}} \rightarrow T_0$  and  $\tau$  are characteristic to flip-flop

→  $\frac{T_0}{T_c} \rightarrow$  prob. that input changes at a bad time

Synchronizers:

→ asynchronous inputs like human inputs are inevitable in larger systems  $\rightarrow$  needs handling to prevent metastability

→ a synchronizer receives async. input  $D$  and  $CLK$ , produces  $Q$  in bounded time, the output has a valid logic level with near certainty (if  $D$  stable,  $Q = D$ , else choose HIGH or LOW)


→ in the image,  $F_1$  samples  $D$  on the rising edge of  $CLK$  (during aperture, momentarily metastable)

→ Over the clock period,  $D_2$  resolves,  $F_2$  samples  $D_2$ , we get a good output  $Q$

→ synchronizer fails when  $Q$  becomes metastable  $\rightarrow t_{res} > T_c - t_{setup}$

$\rightarrow P(\text{failure}) = \frac{T_0}{T_c} e^{-\frac{T_c - t_{setup}}{\tau}}$ ,  $P(\text{failure})/\text{sec} = N \frac{T_0}{T_c} e^{-\frac{T_c - t_{setup}}{\tau}}$   
 $\uparrow$  times  $D$  changes per second  
 (MTBF)

 → mean time between failures usually measures system reliability  $\Rightarrow MTBF = \frac{1}{P(\text{failure}/\text{sec})} = \frac{T_c}{N T_0} e^{\frac{T_c - t_{setup}}{\tau}}$



synchronizer circuit

Some notes on parallelism (pipelining will be introduced)

Token  $\rightarrow$  group of inputs processed to produce group of outputs

Latency  $\rightarrow$  time for 1 token to pass from start to end

Throughput  $\rightarrow$  number of tokens per unit time

Spatial parallelism: multiple copies of hardware, Temporal parallelism (pipelining): task broken into stages, multiple tasks spread across stages  $\rightarrow$  different task in each stage at once

$\rightarrow$  assume a latency  $L$  for a nonparallel task with a throughput of  $1/L$ . With  $N$  copies of HW, it becomes  $N/L$ , which is the ideal case for temporal par. too, but in practice, you get  $1/L_1 \leftarrow$  longest latency for a step

$\rightarrow$  Exam practicality: Prof. Muttu hasn't made a timing task yet, but they do come up in older exams

Nice trivial question! (P515), we're looking at e)

$\rightarrow$  in general, I would focus on the basics, less on skew/synchronizers


next section: Verilog!

$\rightarrow$  this may be asked: Verilog is not a programming language, it is a HDL (hardware description language) to allow for synthesis of digital circuits, but it often features similar syntax

$\rightarrow$  a module is a HW block that needs defined inputs/outputs

$\rightarrow$  Behavioral Verilog: using logical operators to describe what a module does

 $\rightarrow$  Structural Verilog: gate-level description at the bottom level, at a higher level it is about building modules using instances of modules



$\rightarrow$  you start with name and listing I/O

$\rightarrow$  the assign LHS = RHS statement is used for CL outside always statements


$\rightarrow \neg \rightarrow$  NOT,  $\& \rightarrow$  AND,  $| \rightarrow$  OR,  $\sim \& \rightarrow$  NAND,  $\sim | \rightarrow$  NOR,  $\wedge \rightarrow$  XOR,  $\sim \wedge \rightarrow$  XNOR

$\rightarrow$  Verilog signals (individual bits of variables) can be set to 0, 1, Z, X  
floating unknown

$\rightarrow$  Simulation: checking modules for logical correctness

$\rightarrow$  Synthesis: HDL code is transformed to a netlist describing hardware produced

 $\rightarrow$  code may be simplified during synthesis, there is a schematic output like so:




$\rightarrow$  a top module is the main piece of hardware, can consist of CL blocks, registers, FSMs

$\rightarrow$  CL: bitwise operators act on single-bit signals or multi-bit busses

```
module inv (input [3:0] a,
            output [3:0] y);
    assign y = ~a;
endmodule
```

 $a[3:0] \leftarrow$  4-bit bus, given in little-endian order ( $a[3]$  is MSB,  $a[0]$  is LSB)  
 $a[0:3] \leftarrow$  big-endian, also permitted  
 $\rightarrow$  just be consistent



```
module sillyfunction (input a, b, c,
                      output y);
    assign y = ~a & ~b & ~c |
              a & ~b & ~c |
              a & ~b & c;
endmodule
```

| Verilog Operator | Name                      | Functional Group |
|------------------|---------------------------|------------------|
| [ ]              | bit-select or part-select |                  |
| ( )              | parenthesis               |                  |
| !                | logical negation          | logical          |
| ~                | negation                  | bit-wise         |
| &                | reduction AND             | reduction        |
|                  | reduction OR              | reduction        |
| ~&               | reduction NAND            | reduction        |
| ~                | reduction NOR             | reduction        |
| ^                | reduction XOR             | reduction        |
| ~^ or ^^         | reduction XNOR            | reduction        |
| +                | unary (sign) plus         | arithmetic       |
| -                | unary (sign) minus        | arithmetic       |
| { }              | concatenation             | concatenation    |
| { { }            | replication               | replication      |
| *                | multiply                  | arithmetic       |
| /                | divide                    | arithmetic       |
| %                | modulus                   | arithmetic       |
| +                | binary plus               | arithmetic       |
| -                | binary minus              | arithmetic       |
| <<               | shift left                | shift            |
| >>               | shift right               | shift            |
| >                | greater than              | relational       |
| >=               | greater than or equal to  | relational       |
| <                | less than                 | relational       |
| <=               | less than or equal to     | relational       |
| ==               | case equality             | equality         |
| !=               | case inequality           | equality         |
| &                | bit-wise AND              | bit-wise         |
| ^                | bit-wise XOR              | bit-wise         |
|                  | bit-wise OR               | bit-wise         |
| &&               | logical AND               | logical          |
|                  | logical OR                | logical          |
| ?:               | conditional               | conditional      |

```

module gates(input [3:0] a, b,
            output [3:0] y1, y2,
                    y3, y4, y5);

/* Five different two-input logic
gates acting on 4 bit busses */
assign y1 = a & b; // AND
assign y2 = a | b; // OR
assign y3 = a ^ b; // XOR
assign y4 = ~(a & b); // NAND
assign y5 = ~(a | b); // NOR
endmodule

```

→ you know the code, the assign statements we saw are continuous, end with ;

→ when inputs on RHS change, LHS recomputed

→ Verilog comments are exactly like Java

→ white space is irrelevant; module names can't begin with numbers, vars. are case-sensitive

reduction operators → using the operators we just introduced in a unary way

conditional assignment: you know this as the ternary operator

```

module mux4(input [3:0] d0, d1, d2, d3,
            input [1:0] s,
            output [3:0] y);

assign y = s[1] ? (s[0] ? d3 : d2)
           : (s[0] ? d1 : d0);
endmodule

```

i did this for Lab 5

```

module and8(input [7:0] a,
            output y);

assign y = &a;

// &a is much easier to write than
// assign y = a[7] & a[6] & a[5] & a[4] &
// a[3] & a[2] & a[1] & a[0];
endmodule

```

```

module fulladder(input a, b, cin,
                output s, cout);

wire p, g;

assign p = a ^ b;
assign g = a & b;

assign s = p ^ cin;
assign cout = g | (p & cin);
endmodule

```

boolean equations for this full adder:  $P = A \oplus B$ ,  $G = A \cdot B$ ,  $S = P \oplus C_{in}$ ,  $C_{out} = G + P \cdot C_{in}$

→ the continuous assign statements are concurrent → for CL, order doesn't matter

→ wires are declared to hold internal vars. like P and G, they only need to be declared for

multi-bit busses but are good practice

Numbers: (the book won't tell you this: variables can have the data types integer and real → Example: real seven = 7.00;)

Generally: number format:  $N$  <sup>base</sup> <sub>size in bits</sub> value, busses: 'b → binary, 'o → octal, 'd → decimal, 'h → hex

→ size can be omitted; then, a number is assumed to have as many bits as its expression

Table 4.5 Verilog AND gate truth table with z and x

| A | B |   |   |   |
|---|---|---|---|---|
|   | 0 | 1 | z | x |
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | x | x |
| z | 0 | x | x | x |
| x | 0 | x | x | x |

→ you can see x as "should not happen"

Bit Swizzling:  $\text{assign } y = \{2:1, 3:d[0], c[0], 3'b10\}$

you can push z

```

module tristate(input [3:0] a,
                input en,
                output [3:0] y);

assign y = en ? a : 4'bz;
endmodule

```

→  $\{3\}$  concatenates busses and bits → example:  $\{3(d[0])\}$  copies d[0] thrice (incl constants)

Delays: ignored in synthesis; used in simulation and testing → ensure timing is correct

→ of course, electrical factors in gate delays cannot be considered

```

`timescale 1ns/1ps

module example(input a, b, c,
               output y);
wire ab, bb, cb, n1, n2, n3;

assign #1 n1 = a & b & c;
assign #2 n2 = a & bb & cb;
assign #2 n3 = a & bb & c;
assign #4 y = n1 | n2 | n3;
endmodule

```

→ timescale is necessary in a file i believe, format: 'timescale unit/precision'

→ here: every unit is 1ns, sim. has 1ps precision

→ # indicates number of units of delay → here: and → 2ns delay, or → 4ns delay

→ can be placed in assign, non-blocking, blocking assignments

structural modelling:

→ the book actually employs bad practice for instantiation:

→ good practice: submodule name (.input1(i), .output1(o))  
example → mux2 lowmux(.d0(d0), .d1(d1), .s(s[0]), .y(low));

(example)

→ accessing parts of busses: use array notation following your endian format → d0[7:4]

```

module mux2(input [3:0] d0, d1,
            input s,
            output [3:0] y);
tristate t0(d0, s, y);
tristate t1(d1, s, y);
endmodule

```

you can operate in restrictions

```

module mux4(input [3:0] d0, d1, d2, d3,
            input [1:0] s,
            output [3:0] y);

wire [3:0] low, high;

mux2 lowmux(d0, d1, s[0], low);
mux2 highmux(d2, d3, s[0], high);
mux2 finalmux(low, high, s[1], y);
endmodule

```

3 instances of mux2

```

module mux2_8(input [7:0] d0, d1,
              input s,
              output [7:0] y);

mux2 lsbmux(d0[3:0], d1[3:0], s, y[3:0]);
mux2 msbmux(d0[7:4], d1[7:4], s, y[7:4]);
endmodule

```



## Sequential Blocks:

```
module flop (input      clk,
             input  [3:0] d,
             output reg [3:0] q);

    always @ (posedge clk)
        q <= d;
endmodule
```

→ register logic is performed using always statements (always @ (sensitivity list) !)

→ signals keep their values unless an event in the sensitivity list occurs

→ usually it is a clock, as in this case → posedge: rising edge, negedge: falling edge

→ we don't use assign statements here, those are for CL blocks outside of always statements

→ instead, we use the nonblocking assignment (<=), which is used for seq. logic and runs concurrently (in order) unlike =

→ all signals on the LHS of always statements must be declared a register → example: output reg [3:0] q

example: resettable register, allowing for both sync. and async. reset  
(2 modules)

→ multiple elements in an always sens. list are separated by a comma or "or"

→ you will see, we have if statements, for loops, while loops ...

## Synchronizer:

```
module sync (input      clk,
             input  [3:0] d,
             output reg [3:0] q);

    reg n1;

    always @ (posedge clk)
        begin
            n1 <= d;
            q <= n1;
        end
endmodule
```


→ begin and end are necessary in any statement or block

that makes more than one assignment, good practice otherwise
 
## Latch:

```
module latch (input      clk,
              input  [3:0] d,
              output reg [3:0] q);

    always @ (clk, d)
        if (clk) q <= d;
endmodule
```




```
module flopr (input      clk,
              input      reset,
              input  [3:0] d,
              output reg [3:0] q);

    // asynchronous reset
    always @ (posedge clk, posedge reset)
        if (reset) q <= 4'b0;
        else      q <= d;
endmodule

module flopr (input      clk,
              input      reset,
              input  [3:0] d,
              output reg [3:0] q);

     // synchronous reset
    always @ (posedge clk)
        if (reset) q <= 4'b0;
        else      q <= d;
endmodule
```



→ always @ (clk, d) recomputes statements inside whenever clk or d changes

→ always @ (\*) recomputes the statements inside whenever any signal on RHS of = or <= changes

→ blocking assignment (=) used for CL in always blocks, they run sequentially in-order

→ always blocks mostly for sequential blocks, but can behaviorally describe CL if the sens. list responds to all input changes and the body gives outputs in all cases

→ the book calls always blocks "always/process statements"

→ case and if can only be used in always or initial blocks (initial does not synthesize and is used for testbenches)

```
module sevenseg (input      [3:0] data,
                 output reg [6:0] segments);

    always @ (*)
        case (data)
            // abc_defg
            0: segments = 7'b111_1110;
            1: segments = 7'b011_0000;
            2: segments = 7'b110_1101;
            3: segments = 7'b111_1001;
            4: segments = 7'b011_0011;
            5: segments = 7'b101_1011;
            6: segments = 7'b101_1111;
            7: segments = 7'b111_0000;
            8: segments = 7'b111_1111;
            9: segments = 7'b111_1011;
            default: segments = 7'b000_0000;
        endcase
endmodule
```

→ case checks value of an input (here data) in base 10

→ if-else statements can be made like in regular programming, just follow the begin/end rules


→ case\_z includes don't cares from T1's as ?

→ rule in always blocks: don't assign to the same signal more than once

```
module priority_case2 (input      [3:0] a,
                     output reg [3:0] y);

    always @ (*)
        case2 (a)
            4'b1111: y = 4'b1000;
            4'b0111: y = 4'b0100;
            4'b0011: y = 4'b0010;
            4'b0001: y = 4'b0001;
            default: y = 4'b0000;
        endcase
endmodule
```

sign. control:

 



# FSM:

## Verilog (divides CLK by 3)

```
module divideby3FSM(input clk,
                    input reset,
                    output y);
    reg [1:0] state, nextstate;


    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;

    // state register
    always @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else state <= nextstate;

    // next state logic
    always @(*)
        case (state)
            S0: nextstate = S1;
            S1: nextstate = S2;
            S2: nextstate = S0;
            default: nextstate = S0;
        endcase


    // output logic
    assign y = (state == S0);
endmodule
```

 - parameter statements are used to define constants and are standard for any FSM state
- default in case needed to fulfill our def. of combinational for next state logic
- notice the equality comparison == or inequality != with strict versions === and !==


 
## FSM Example 2: Recall the Smiling Snail

- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it
- The snail smiles whenever the last four digits it has crawled over are 1101
- Design Moore and Mealy FSMs of the snail's brain



## Verilog (Moore-style)

```
module patternMoore(input clk,
                    input reset,
                    input a,
                    output y);
    reg [2:0] state, nextstate;

    parameter S0 = 3'b000;
    parameter S1 = 3'b001;
    parameter S2 = 3'b010;
    parameter S3 = 3'b011;
    parameter S4 = 3'b100;

    // state register
    always @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else state <= nextstate;

    // next state logic
    always @(*)
        case (state)
            S0: if (a) nextstate = S1;
                else nextstate = S0;
            S1: if (a) nextstate = S2;
                else nextstate = S0;
            S2: if (a) nextstate = S2;
                else nextstate = S3;
            S3: if (a) nextstate = S4;
                else nextstate = S0;
            S4: if (a) nextstate = S2;
                else nextstate = S0;
            default: nextstate = S0;
        endcase

    // output logic
    assign y = (state == S4);
endmodule
```

## Verilog (Mealy style)

```
module patternMealy(input clk,
                    input reset,
                    input a,
                    output y);
    reg [1:0] state, nextstate;

    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;
    parameter S3 = 2'b11;

    // state register
    always @(posedge clk, posedge reset)
        if (reset) state <= S0;
        else state <= nextstate;

    // next state logic
    always @(*)
        case (state)
            S0: if (a) nextstate = S1;
                else nextstate = S0;
            S1: if (a) nextstate = S2;
                else nextstate = S0;
            S2: if (a) nextstate = S2;
                else nextstate = S3;
            S3: if (a) nextstate = S1;
                else nextstate = S0;
            default: nextstate = S0;
        endcase

    // output logic
    assign y = (a & state == S3);
endmodule
```

## Parameterizing:

### Verilog

```
module mux2
    #(parameter width = 8)
    (input [width-1:0] d0, d1,
     input [width-1:0] s,
     output [width-1:0] y);
    assign y = s ? d1 : d0;
endmodule
```

default value  
depends on width  
we use output [width-1:0] y;  
passing a variable to decide module's width

```
module mux4_8(input [7:0] d0, d1, d2, d3,
              input [1:0] s,
              output [7:0] y);
    wire [7:0] low, hi;
    mux2 lowmux(d0, d1, s[0], low);
    mux2 hixmap(d2, d3, s[1], hi);
    mux2 outmux(low, hi, s[1], y);
endmodule
```

→ you can instantiate like normal - 8 is default

```
module mux4_12(input [11:0] d0, d1, d2, d3,
               input [1:0] s,
               output [11:0] y);
    wire [11:0] low, hi;
    mux2 #(12) lowmux(d0, d1, s[0], low);
    mux2 #(12) hixmap(d2, d3, s[1], hi);
    mux2 #(12) outmux(low, hi, s[1], y);
endmodule
```

→ need to instantiate with parameter 12

Testbenches: ~ HDL module used to test another module, called Device Under Test (DUT)

→ inputs and expected outputs → test vectors

Simple testbenches: instantiate DUT, apply inputs in initial block, use blocking assignments and delays, then the user manually verifies correct outputs → simulated like any module, not synthesizable

→ example: sillyfunction is a simple 3-input logic function → test vectors

```
module testbench1();
    reg a, b, c;
    wire y;

    // instantiate device under test
    sillyfunction dut(a, b, c, y);

    // apply inputs one at a time
    initial begin
        a = 0; b = 0; c = 0; #10;
        c = 1; #10;
        b = 1; c = 0; #10;
        c = 1; #10;
        a = 1; b = 0; c = 0; #10;
        c = 1; #10;
        b = 1; c = 0; #10;
        c = 1; #10;
    end
endmodule
```